



**Faculty of Engineering and Technology**  
**Department of Electrical and Computer Engineering**  
**DIGITAL INTEGRATED CIRCUITS- ENCS3330**

**HW#4 : TOOL ASSIGNMENT EXPERIMENT-1**

Prepared by  
Arwa Doha – 1190324

Instructor  
Dr. Khader Mohammad  
Eng: Raha Ahmad

BIRZEIT  
Jun– 2023

## Lab work:

### 1) Design, layout, and simulation of CMOS NAND gate:

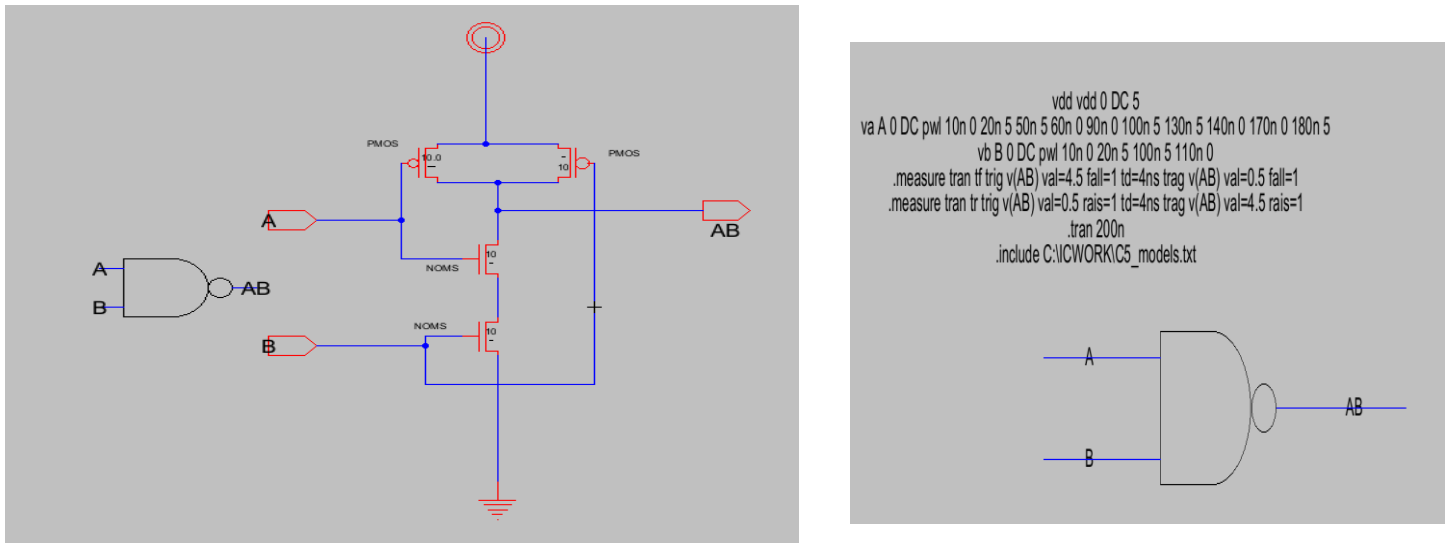


Figure 1.1: the schematic for NAND gate.

 


Figure 1.2: the layout for NAND gate.


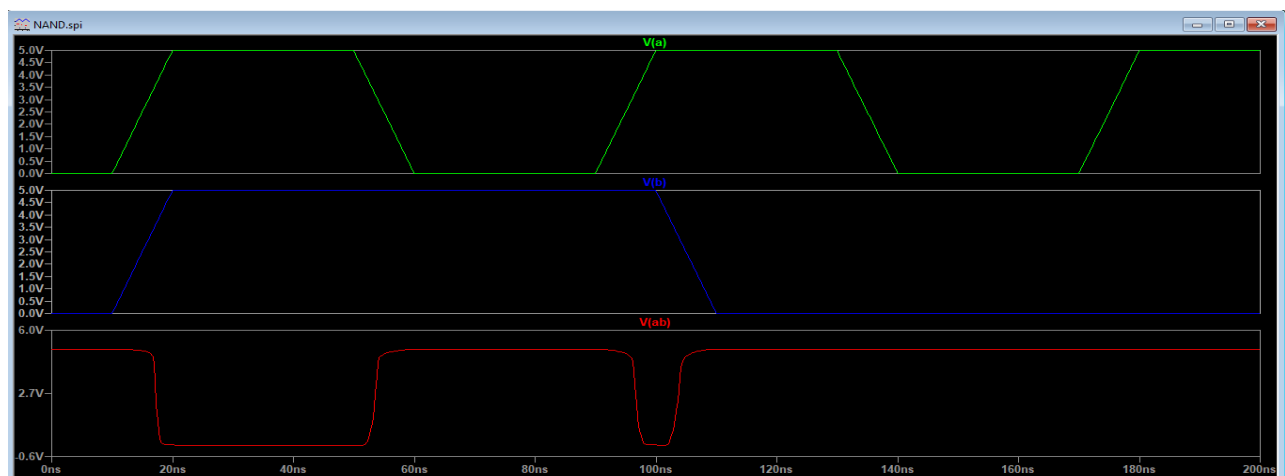
 


Figure 1.3: the symulation for NAND gate.

 2) Design, layout, and simulation of CMOS XOR gate:



```
vdd vdd 0 DC 5
va A 0 DC pwl 10n 0 20n 5 50n 5 60n 0 90n 0 100n 5 130n 5 140n 0 170n 0 180n 5
vb B 0 DC pwl 10n 0 20n 5 100n 5 110n 0
.tran 200n
.include C:\ICWORK\C5_models.txt
```

Figure2.1: the schematic for Xor gate.

 


Figure 2.2: the layout for Xor gate.

 


Figure 2.3: the symulation for Xor gate.

3) Design, layout, and simulation of CMOS Full adder gate using the previous components:

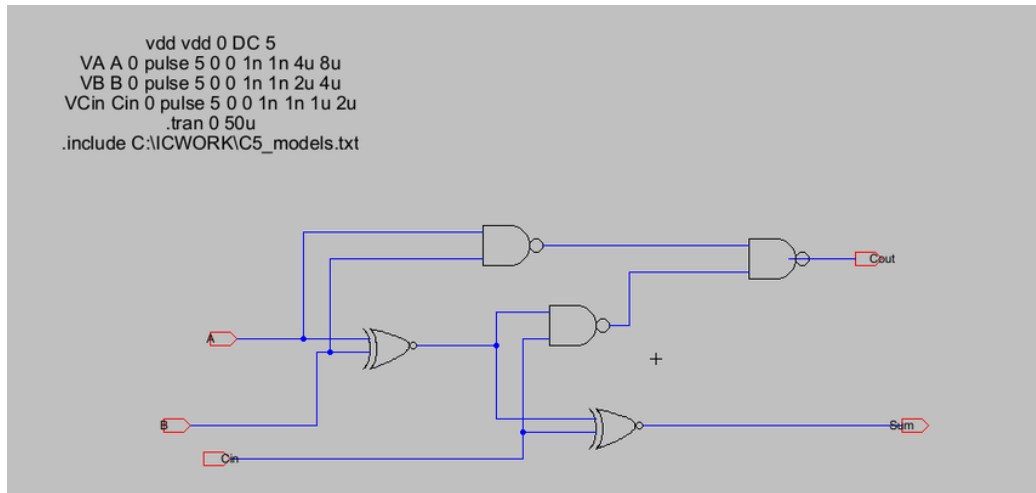


Figure 3.1: the schematic for Full adder.

 


Figure 3.2: layout for Full adder.

 


Figure 3.3: symulation for Full adder.